



**ammini**  
**College of Engineering**

*(Approved by AICTE & Affiliated to Calicut University)*

***DEPARTMENT OF ELECTRICAL & ELECTRONICS  
ENGINEERING***

***ELECTRICAL  
MEASUREMENTS AND  
INSTRUMENTATION LAB***

<b>CLASS</b>	<b>: II YEAR (EEE)</b>
<b>SEMESTER</b>	<b>: IV<sup>th</sup> SEM (EEE)</b>
<b>SUBJECT CODE</b>	<b>: EE09 408 (P)</b>
<b>SUBJECT</b>	<b>: ELECTRICAL MEASUREMENTS AND INSTRUMENTATION</b>




**EE09 408(P): ELECTRICAL MEASUREMENTS AND  
INSTRUMENTATION LAB**

**LIST OF EXPERIMENTS**


<b>Sl.No</b>	<b>Name of Experiment</b>	<b>Page No</b>
1	MEASUREMENT OF RESISTANCE USING WHEATSTONE BRIDGE	03
2	RESISTANCE MEASUREMENT USING KELVINS DOUBLE BRIDGE	07
3	CALIBRATION OF SINGLE PHASE STATIC ENERGY METER	11
4	CALIBRATION OF SINGLE PHASE ENERGY METER BY PHANTOM LOADING WITHOUT USING PHASE SHIFTING TRANSFORMER	17
5	CALIBRATION OF SINGLE PHASE ENERGY METER BY DIRECT LOADING	23
6	MEASUREMENT OF SELF INDUCTANCE, MUTUAL INDUCTANCE AND COUPLING COEFFICIENT OF TRANSFORMER COILS	27
7	EXTENSION OF RANGE OF WATTMETER USING CT& PT	33
8	CALIBRATION OF SINGLE PHASE ENERGY METER BY PHANTOM LOADING USING PHASE SHIFTING TRANSFORMER	37
9	EXTENSION OF RANGE OF AMMETER USING CURRENT TRANSFORMER	41
10	LINEAR VARIABLE DIFFERENTIAL TRANSFORMER MEASUREMENTS	45
11	CALIBRATION OF THREE PHASE STATIC ENERGY METER	49
12	THERMOCOUPLE CHARACTERISTICS	55
13	RTD CHARACTERISTICS	59



### CIRCUIT DIAGRAM

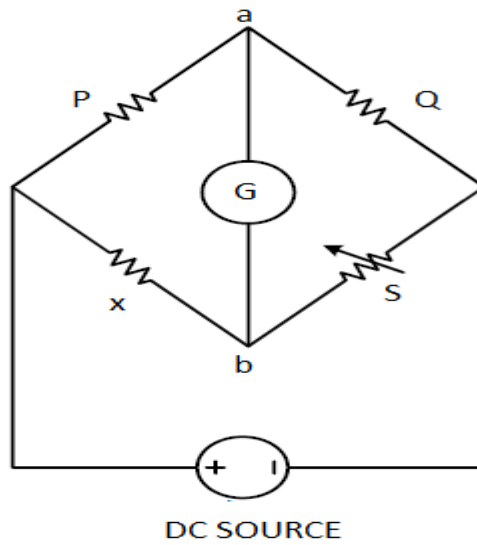

### PORTABLE FORM OF WHEATSTONE BRIDGE

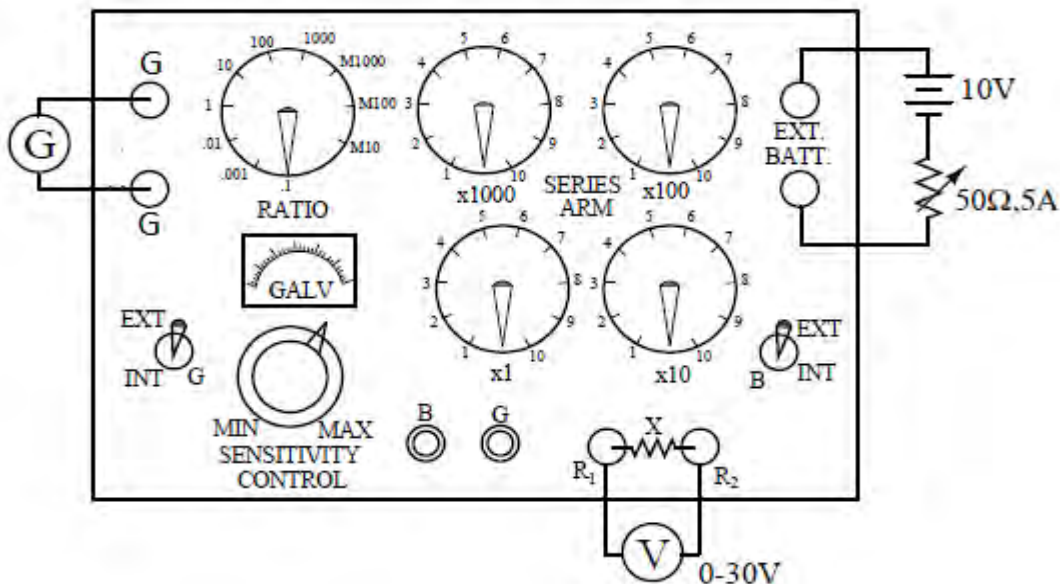

**Expt No:1**

**MEASUREMENT OF RESISTANCE USING WHEATSTONE BRIDGE**

**Aim**

To measure the given medium resistances using Wheatstone bridge.

**Apparatus Required**

Sl.No.	NAME OF THE APPRATUS	RANGE	TYPE	QTY
1	Wheat stone Bridge kit	-	-	1
2	Rheostat	15Ω, 5A	Wire wound	1
3	Voltmeter	0-30V	MC	1
4	Galvanometer	-	-	1
5	DC source	-	-	1

**Principle**

The Wheatstone bridge is the most widely used circuit for precisely measuring resistance by the comparison method. The Wheatstone bridge is designed to be used for precision resistance measurements in the laboratory. Values of resistance from 0.001 to 9,999,000 ohms can be measured with this instrument. When the instrument is used as a Wheatstone bridge, the Ratio Multiplier switch allows selection of seven multipliers from 0.001 to 1,000. Multiplying the reading obtained from the decade dials by the ratio selected yields the value, in ohms, of the unknown resistance. Ratio resistances are accurate to  $\pm 0.05\%$ .

**Procedure**

The given voltmeter(unknown resistance) is connected to the terminal marked X on the bridge. The toggle switches are adjusted for external battery and galvanometer. An external battery is connected to terminals BB through a rheostat. A galvanometer is connected to the terminals marked GG. on the bridge. The P/Q ratio (Multiplier) is suitably selected. The resistance 'S' is varied by varying the four decade resistances (one at a time starting from the highest range) till null deflection is observed in the galvanometer, when the 'B' and 'G' keys are pressed. Adjustments are made till null deflection is obtained, The reading of the 'Multiplier' and

**Tabular Column**

Sl.no	Unknown resistance	P/Q ratio (multiplier)	S <sub>1</sub> (Ω)	S <sub>2</sub> (Ω)	S <sub>3</sub> (Ω)	S <sub>4</sub> (Ω)	S = S <sub>1</sub> +S <sub>2</sub> +S <sub>3</sub> +S <sub>4</sub> (Ω)	Unknown Resistance X=(p/q)*s (Ω)

**Sample Calculation**

$\frac{P}{Q}$  = .....

S<sub>1</sub> = .....

S<sub>2</sub> = .....

S<sub>3</sub> = .....

S<sub>4</sub> = .....

S = S<sub>1</sub>+S<sub>2</sub>+S<sub>3</sub>+S<sub>4</sub> = .....

X = (P/Q)\*S = .....

the four dials of the variable resistance 'S' are noted. The readings are tabulated as shown. The experiment is repeated for rheostat instead of voltmeter.


**Result**

Measured the given voltmeter using Wheatstone bridge.


Resistance of voltmeter =.....

Resistance of Rheostat=.....

**CIRCUIT DIAGRAM**

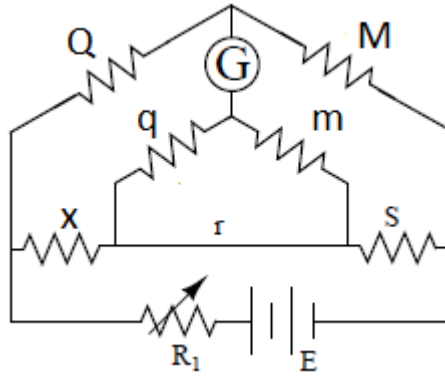

**KELVIN DOUBLE BRIDGE**

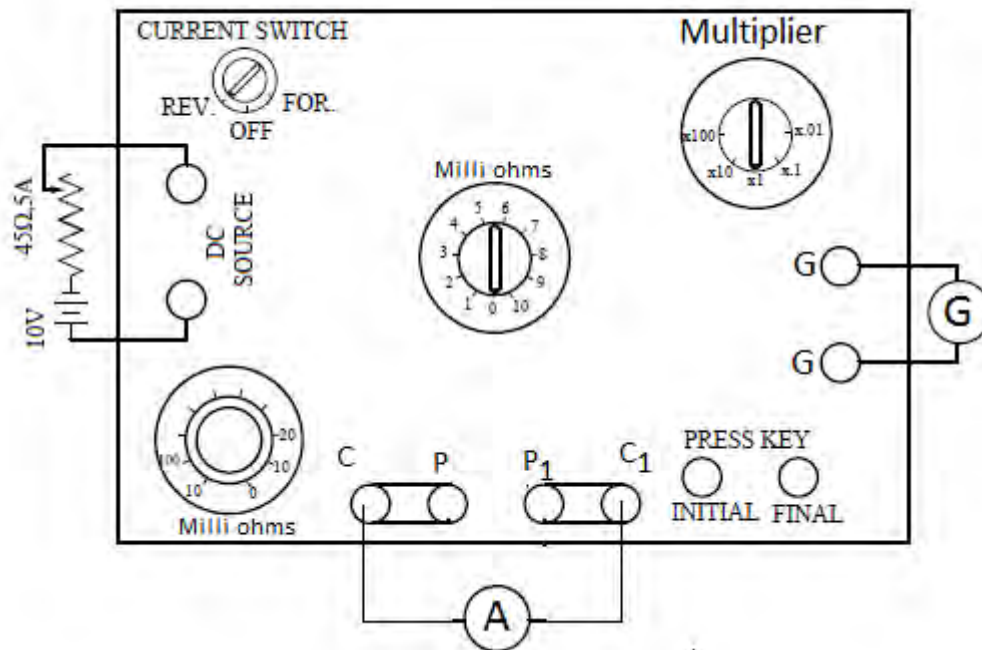



**Expt No:2**

**RESISTANCE MEASUREMENT USING KELVINS DOUBLE BRIDGE**

**Aim**

To measure the resistance of the given ammeter(0-2.5A) using Kelvins double bridge.

**Apparatus Required**

SL.NO	NAME OF THE APPRATUS	RANGE	TYPE	QTY
1	Kelvins Double Bridge	-	-	1
2	D.C source	(0-30V)	DC	1
3	Ammeter	(0-2.5A)	MC	1
4	Galvanometer	-	-	1
5	Rheostat	45,5A	Wire wound	-

**Principle**

This method is the best available for precise measurement of low resistances(less than 1). In the figure 'X' is the low resistance to be measured and 'S' is a standard variable resistance of the same order of magnitude, M,Q, p and q are four non-inductive resistances, one pair of which are variable. These are connected to form two sets of ratio arms, which are used for range selection. The ratio Q/M is kept same as q/m ratio along with 'S' being varied till null deflection of the galvanometer is obtained.

$$\text{Then } \frac{Q}{M} = \frac{X}{S} = \frac{q}{m}$$

**Procedure**

Connections are made as shown in the figure. Choose a suitable range multiplier. Set the current switch in forward position. Press the galvanometer initial key first and adjust main dial and slide wire to get null deflection in the galvanometer. Then press the galvanometer final

**Tabular Column**

SI No.	Unknown Resistance	Remarks	Range Multiplier	S <sub>1</sub> (mΩ)	S <sub>2</sub> X10 <sup>-4</sup> (Ω)	S=S <sub>1</sub> +S <sub>2</sub> (Ω)	X (mΩ)	Mean Resistance (mΩ)
1	Ammeter+ leads	Direct						
		Reverse						
2	Leads only	Direct						
		Reverse						

**Sample Calculation** (Set No.....)

*For Direct:*

Range multiplier=.....

S<sub>1</sub>=.....

S<sub>2</sub>=.....

S=S<sub>1</sub>+S<sub>2</sub>=.....

X<sub>1</sub>=(Range Multiplier) X (S)=.....

*For Reverse:*

Range multiplier=.....

S<sub>1</sub>=.....

S<sub>2</sub>=.....

S=S<sub>1</sub>+S<sub>2</sub>=.....

X<sub>2</sub>=(Range Multiplier) X (S)=.....

Mean Resistance X=(X<sub>1</sub>+X<sub>2</sub>)/2=.....

Resistance of ammeter= (Resistance of ammeter + leads) - (Resistance of leads alone)=.....

key and check whether the galvanometer reads null deflection. If not, adjust the dial readings to get null deflection. The readings of the main dial and slide wire are noted down. The current switch is then put to the reverse position. This reverses the direction of current in circuit. The main dial and slide wire are adjusted to get null deflection and the readings are noted again. The mean of the two is taken as the correct value. This is done to eliminate errors due to thermal effect. The ammeter is then disconnected and the resistance of the connecting leads alone is measured using the same method. The experiment is repeated with different values of range multiplier. The readings are tabulated as shown.


Resistance of ammeter = (Resistance of ammeter + leads) - (Resistance of leads alone)

### **Result**

Measured the resistance of the given ammeter using Kelvins double bridge.

Resistance of given ammeter =

**CIRCUIT DIAGRAM**

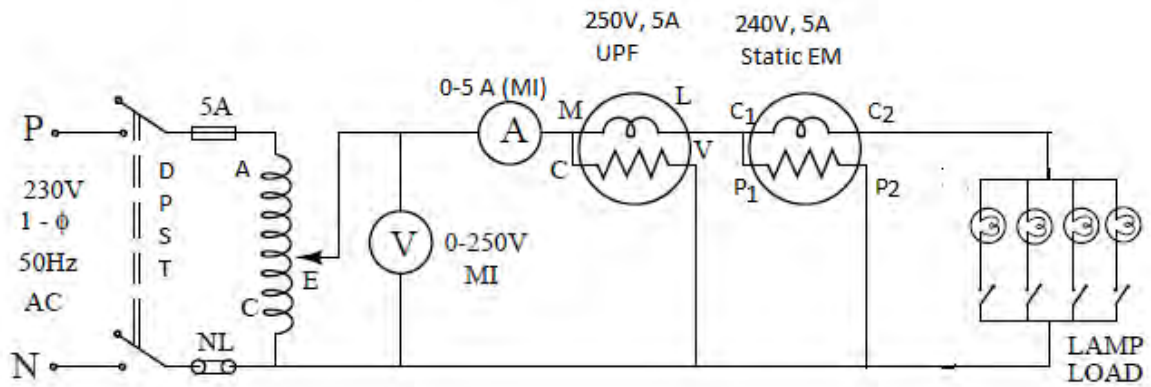

**Tabular Column**

Sl. No.	Volt meter Reading (V)	Ammeter Reading (A)	Wattmeter Reading (W)	Time for 5 Impulses $t_1$ (s)	Time for 1 Impulse $t_2$ (s)	Indicating Reading IR(ws)	True Reading TR (ws)	Error IR-TR (ws)	%Error

**Expt No:3**

**CALIBRATION OF SINGLE PHASE STATIC ENERGY METER**

**Aim**


To calibrate the given single phase static energy meter at unity power factor by direct loading.

**Apparatus Required**


SI.NO	NAME OF THE APPRATUS	RANGE	TYPE	QTY
1	Autotransformer	0-270 V	-	1
2	Ammeter	0-5A	MI	1
3	Voltmeter	0-300V	MI	1
4	Wattmeter	250V, 5A	UPF	1
5	Energy Meter	240V, 5A 3200 imp/kWhr	Static	1
6	Lamp Load	-	-	-

### Sample Graph

*Error Curve*

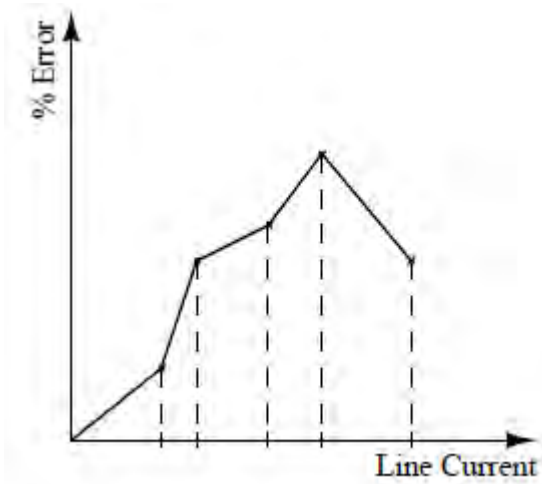

*Calibration Curve*

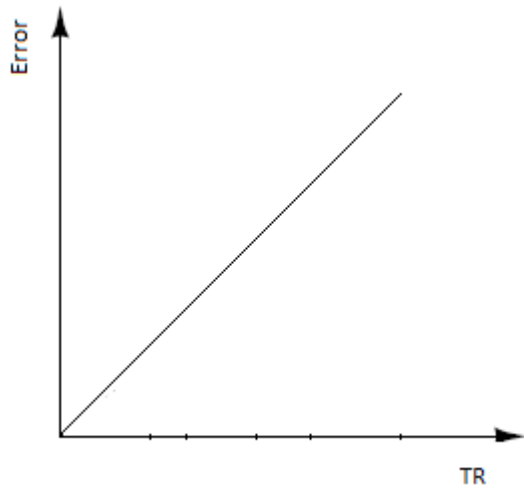

## **Principle**

An energy meter is an instrument used to measure electrical energy. It keeps a record of the total energy consumed in a circuit during a particular period. It is an integrating type of instrument. Calibration involves comparing the energy measured by an energy meter with a standard instrument. The standard chosen here is a wattmeter. Since the wattmeter measures only the power, it has to be multiplied with time to get the energy reading. The readings are then compared to find the error in the energy meter.

Calibration can be done either by direct loading or phantom loading. In direct loading both the current and pressure coils are fed from the same supply at rated voltage. Energy meters of high rating when tested by direct loading would involve large amount of power. Such meters are thus tested using phantom loading, wherein the pressure coil is supplied from rated supply and current coil circuit from a separate low voltage supply.

## **Procedure**

Connections are made as shown in the connection diagram. The supply is switched on, keeping the autotransformer in the minimum position. The autotransformer is then varied to get the rated voltage. The lamp load is then switched on and the ammeter reading adjusted for a small value of current. The corresponding readings of voltmeter, ammeter and wattmeter are noted down. The time for five impulse of the energy meter disc is also noted. The experiment is repeated in steps adding loads till the rated current of the energy meter is reached. The true energy and indicated energy is evaluated and the error found out. The error curve and calibration curve are then plotted as shown.

**Sample calculation**( Set No.....)

Energy meter constant  $k = \dots\dots\dots$

Voltmeter reading (V) =  $\dots\dots\dots$

Ammeter reading (I) =  $\dots\dots\dots$

Time for 5 impulse of energy meter( $t_1$ ) =  $\dots\dots\dots$

Time for 5 impulse of energy meter ( $t_2$ ) =  $\frac{t_1}{5} = \dots\dots\dots$

Indicated energy for 1 impulse of energy meter (IR) =  $\frac{1}{K} * 60 * 60 * 1000 = \dots\dots\dots$

Wattmeter reading (W) =  $\dots\dots\dots$

True energy for ' $t_2$ ' seconds (TR) =  $W \times t_2 = \dots\dots\dots$

Error =  $IR - TR$


% Error =  $\frac{IR - TR}{IR} * 100 = \dots\dots\dots$




**Result**

Calibrated the given single phase static energy meter at unity power factor by direct loading.

**CIRCUIT DIAGRAM FOR UPF (FIG 1)**

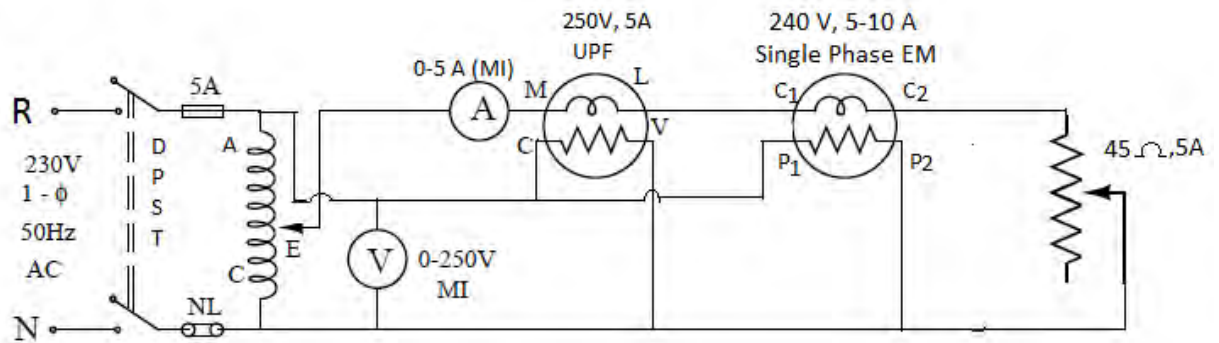

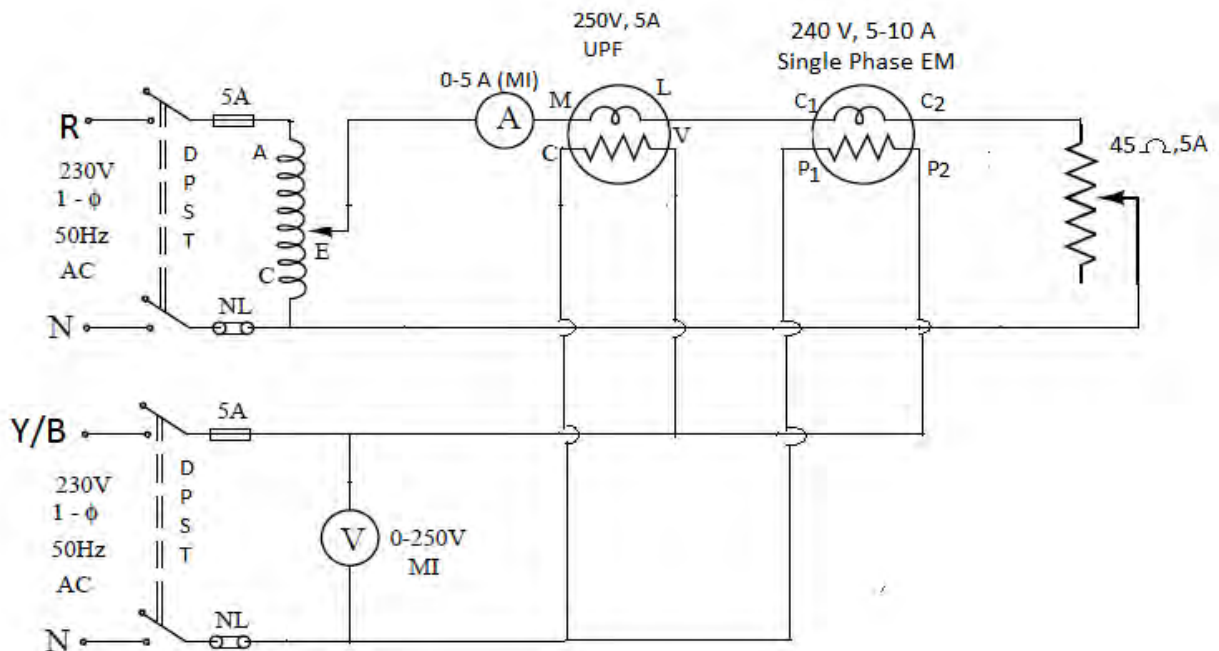**CIRCUIT DIAGRAM FOR 0.5 LAG/LEAD (FIG 2)**



**Expt No:4**

**CALIBRATION OF SINGLE PHASE ENERGY METER BY PHANTOM  
LOADING WITHOUT USING PHASE SHIFTING TRANSFORMER**

**Aim**

To calibrate single phase energy meter by phantom loading without using phase shifting transformer

**Apparatus Required**

Sl.No.	NAME OF THE APPRATUS	RANGE	TYPE	QTY
1	Autotransformer	0-270 V	Single Phase	1
2	Ammeter	0-5A	MI	1
3	Voltmeter	0-300V	MI	1
4	Wattmeter	300V, 10A	UPF	1
5	Energy meter	240V,5-10A	Single Phase	1
6	Resistive Load	45Ω, 5A	Wire Wound	1

**Tabular Column**

*For UPF:*

SI No.	Voltmeter Reading (V)	Ammeter Reading (A)	Wattmeter Reading (W)	Time for 5 Revolution( $t_1$ ) (s)	Time for 1 Revolution ( $t_2$ ) (s)	Indicative Reading IR (W)	True Reading TR (W)	Error	%Error

*For 0.5 lag:*

SI No.	Voltmeter Reading (V)	Ammeter Reading (A)	Wattmeter Reading (W)	Time for 5 Revolution( $t_1$ ) (s)	Time for 1 Revolution ( $t_2$ ) (s)	Indicative Reading IR (W)	True Reading TR (W)	Error	%Error

*For 0.5 lead:*

SI No.	Voltmeter Reading (V)	Ammeter Reading (A)	Wattmeter Reading (W)	Time for 5 Revolution( $t_1$ ) (s)	Time for 1 Revolution ( $t_2$ ) (s)	Indicative Reading IR (W)	True Reading TR (W)	Error	%Error

## **Principle**

When an energy meter is designed for high current loads, it is uneconomical to arrange such loads for testing purposes as it involves a considerable waste of time and power. To avoid this problem "phantom" loading is done.

In phantom loading, pressure coil is excited from normal supply voltage and current coil is excited from a separate low voltage supply. The low impedance of current coil circuit makes it possible to circulate the required current even with low supply voltage.

## **Procedure**

For testing energy meter at upf condition connections are done as shown in fig 1. Keep the autotransformer position in minimum and loading rheostat position in maximum. Supply is given and apply rated voltage across pressure coil of energy meter and wattmeter. Current in the current coil of the circuit is adjusted by varying auto transformer. First adjust auto transformer to low value of current (say 1A) and increase the current to rated current (say up to 5A). The voltmeter, ammeter, wattmeter and time for 5 revolution of energy meter are noted for various loads current.

For a power factor of 0.5, connections are made as shown in figure2. Keep the autotransformer position in minimum. The current coil of wattmeter and energy meter is connected in series to R-phase and pressure coil to Y-phase for lead and B-phase for lag. Supply is given and applies rated voltage across pressure coil of energy meter and wattmeter. If the wattmeter reads negative the pressure coil connections are interchanged. Current in the current coil of the circuit is adjusted by varying auto transformer. First adjust auto transformer to low value of current (say 1A) and increase the current to rated current (say up to 5A). The voltmeter, ammeter, wattmeter and time for 5 revolution of energy meter are noted for various loads current. Calculate indicating reading, true reading, error and %error. Then plot error and calibration curve.

**Sample calculation** (Set No.....)

Energy meter constant  $k = \dots\dots\dots$

Voltmeter reading (V) =  $\dots\dots\dots$

Ammeter reading (I) =  $\dots\dots\dots$

Time for 5 revolutions of energy meter disc ( $t_1$ ) =  $\dots\dots\dots$

Time for 5 revolutions of energy meter disc ( $t_2$ ) =  $\frac{t_1}{5} = \dots\dots\dots$

Indicated energy for 1 revolutions of energy meter disc (IR) =  $\frac{1}{K} * 60 * 60 * 1000 = \dots\dots\dots$

Wattmeter reading (W) =  $\dots\dots\dots$

True energy for 't<sub>2</sub>' seconds (TR) =  $W \times t_2 = \dots\dots\dots$


Error =  $IR - TR$

% Error =  $\frac{IR - TR}{IR} * 100 = \dots\dots\dots$

## **Result**


Calibrated single phase energy meter by phantom loading without using phase shifting transformer.

### CIRCUIT DIAGRAM

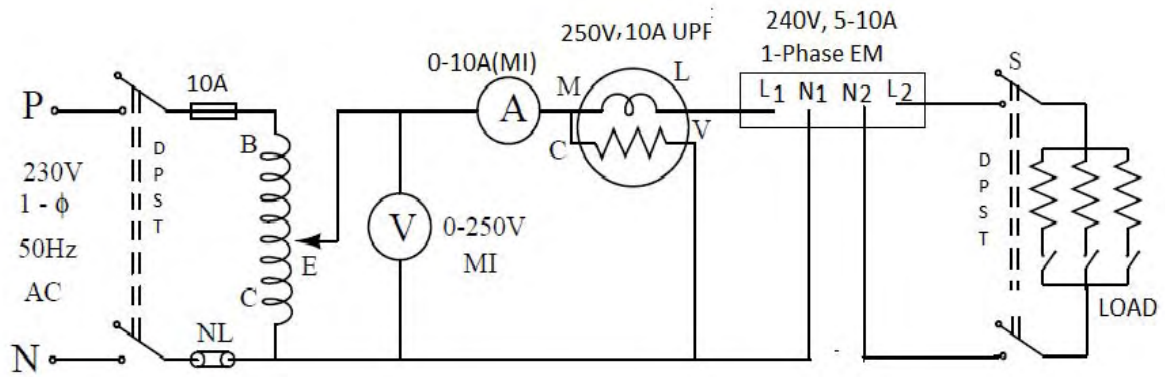


### Sample Graph

Calibration curve

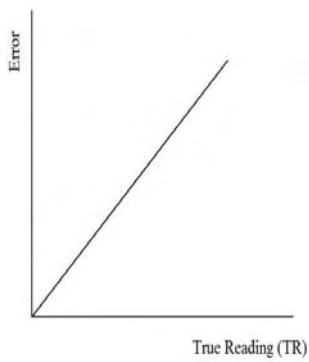

Error Curve

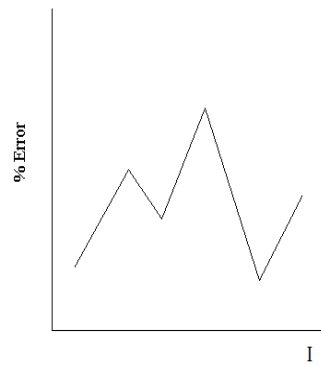



**Expt No:5**

**CALIBRATION OF SINGLE PHASE ENERGY METER BY DIRECT  
LOADING**

**Aim**

To calibrate the single phase energy meter by direct loading at unity power factor .

**Apparatus Required**

SL.NO	NAME OF THE APPRATUS	RANGE	TYPE	QTY
1	Autotransformer	0-270 V	-	1
2	Ammeter	0-5A	MI	1
3	Voltmeter	0-300V	MI	1
4	Wattmeter	250V, 5A	UPF	1
5	Energy Meter	240V, 5A 1800 rev/kWhr	Dynamic	1
6	Load	-	Resistive	-

**Principle**

In order to check the calibration of a single phase energy meter, the reading of the energy meter is compared with that of a standard instrument. For determining the true energy consumption, a standard wattmeter and an accurate stopwatch is used. From the calculated true energy, the error and the percentage error in the energy meter reading is determined.

In direct loading, the current coils of the energy meter and wattmeter are connected to a single phase supply in series with the loading device (say rheostat) whereas the pressure coils are connected directly to the supply. The loading device is adjusted to get the required current. Then the energy consumption is determined by observing the time for a fixed number (say N) of revolutions. The true energy is calculated from the wattmeter reading and the time indicated by the stopwatch.

**Tabular Column**

SI No.	Voltmeter Reading (V)	Ammeter Reading (A)	Wattmeter Reading (W)	Time for 5 Revolution( $t_1$ ) (s)	Time for 1 Revolution ( $t_2$ ) (s)	Indicative Reading IR (W)	True Reading TR (W)	Error	%Error

**Sample calculation** (Set No.....)

Energy meter constant K = .....

Voltmeter reading (V) = .....

Ammeter reading (I) = .....

Time for 5 revolutions of energy meter disc ( $t_1$ ) = .....

Time for 5 revolutions of energy meter disc ( $t_2$ ) =  $\frac{t_1}{5}$  = .....

Indicated energy for 1 revolutions of energy meter disc (IR) =  $\frac{1}{K} * 60 * 60 * 1000$  = .....

Wattmeter reading (W) = .....

True energy for ' $t_2$ ' seconds (TR) =  $W \times t_2$  = .....

Error =  $IR - TR$

%Error =  $\frac{IR - TR}{IR} * 100$  = .....

## **Procedure**


The connections are done as shown in the circuit diagram. Adjust the auto transformer to minimum position. Supply is switched on and rated voltage is applied. Remove the loads completely. The current is varied using loading rheostat till the rated current step by step. The ammeter reading, voltmeter reading, wattmeter reading and time for 5 revolutions of energy meter disc are noted in each step. Remove the load step by step. Adjust the auto transformer to minimum position and switch off supply.

## **Result**


Calibrated the single phase energy meter by direct loading at unity power factor and plotted the graph.

## CIRCUIT DIAGRAM

*For Resistance (R):*

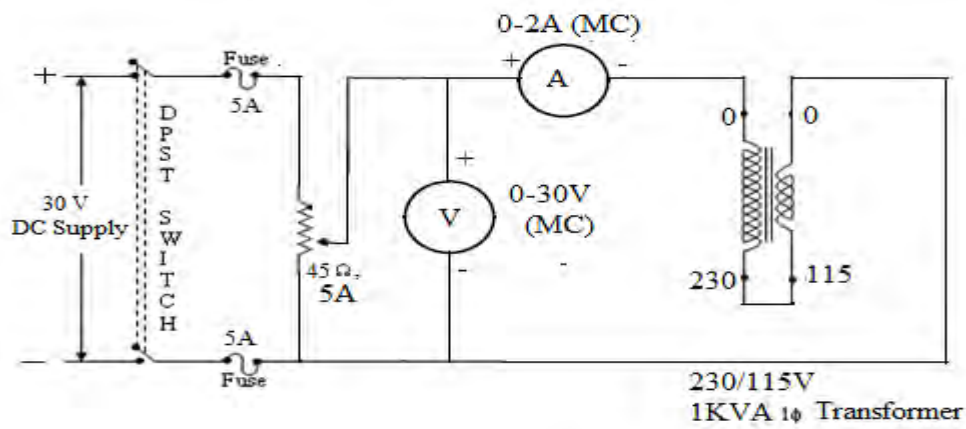

*Aiding Flux Circuit:*

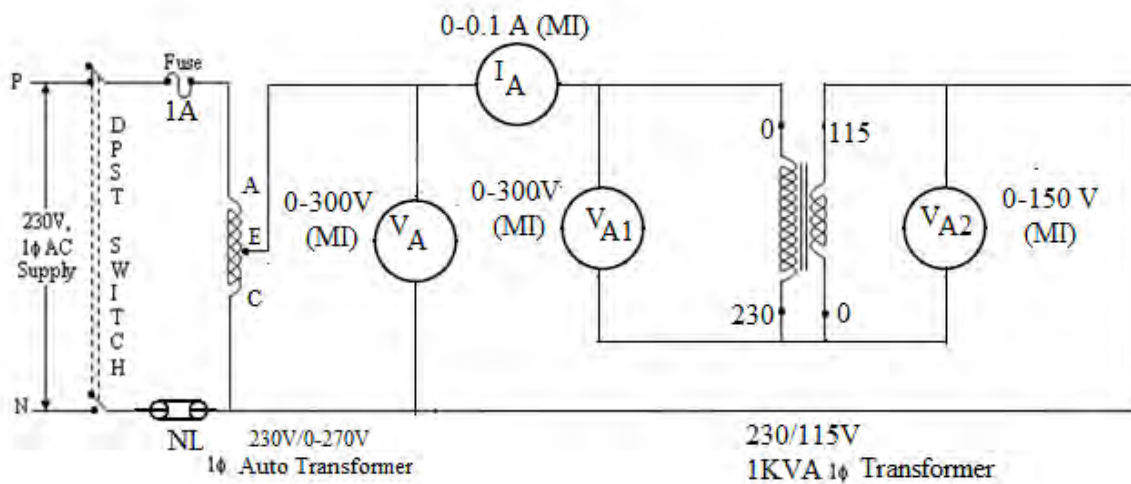

**Expt No:6**

**MEASUREMENT OF SELF INDUCTANCE, MUTUAL INDUCTANCE  
AND COUPLING COEFFICIENT OF TRANSFORMER COILS**


**Aim**

To determine the self inductance, mutual inductance and coupling coefficient of the given iron cored transformer windings.

**Apparatus Required**

S.No.	Apparatus	Range	Type	Quantity
1	Ammeter	(0-0.1)A	MI	1
		(0-2)A	MC	1
2	Voltmeter	(0-300)V	MI	2
		(0-150V)	MI	1
		(0-30V)	MC	
3	Transformer	1KVA, 230/115V Single phase		1
4	Rheostats	45Ω, 5A	Wire Wound	1
5	Auto transformer	230V/(0-270V), single phase	-	1
6	Connecting Wires	2.5sq.mm.	Copper	Few

**Opposing Flux Circuit:**

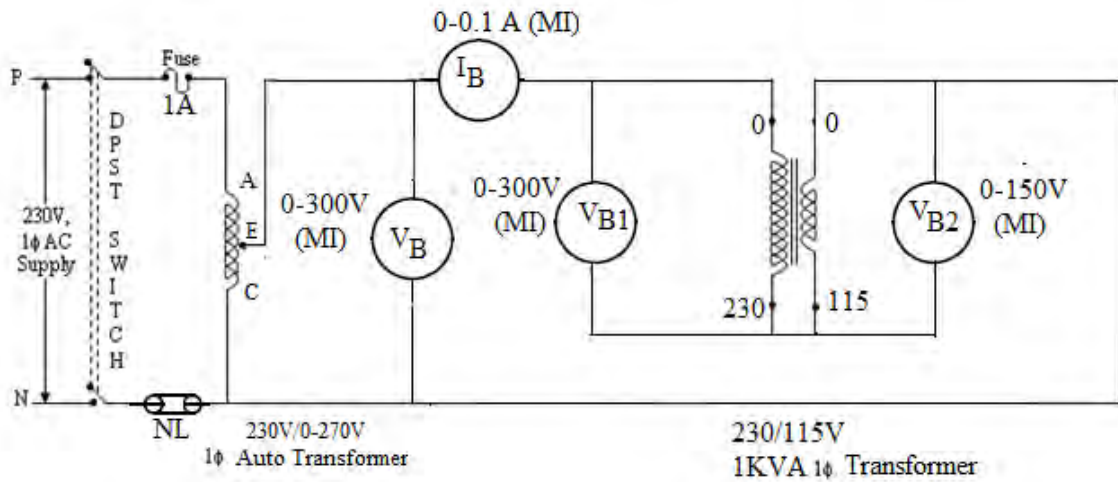

**Tabular Column**

*For Aiding Flux Circuit:*

S.No.	$V_A$ (V)	$V_{A1}$ (V)	$V_{A2}$ (V)	$I_A$ (A)	$V_A = V_{A1} + V_{A2}$ (V)
<b>1</b>					

*For Opposing Flux Circuit:*

S.No.	$V_B$ (V)	$V_{B1}$ (V)	$V_{B2}$ (V)	$I_B$ (A)	$V_B = V_{B1} - V_{B2}$ (V)
<b>1</b>					

## Principle

Inductance is the property of a circuit element by which energy is capable of being stored in a magnetic flux field and any circuit element exhibit the property of inductance is called an inductor.

Self Inductance of a coil is the property by which it opposes any flux through it. Mutual inductance of a coil is the ability to produce an emf in the neighbouring coil by induction, when the current in the first coil changes.

Consider two magnetically coupled coils of self inductance  $L_1$  and  $L_2$ . Let  $M$  be the mutual inductance of the coils connected in series so that flux is produced by current  $I$  through the coils are in the same direction, then the effective inductance

$$L_A = L_1 + L_2 + 2M$$

If coils are connected such that the flux produced by the current in opposite direction, then effective inductance

$$L_B = L_1 + L_2 - 2M$$

Therefore mutual inductance  $M = (L_A - L_B) / 4$

Coupling coefficient  $k = M / ((L_1 L_2)^{1/2})$

In the first case, if  $V_1$  and  $I_1$  are the applied voltage and current, then

$$Z_A = V_1 / I_1 \quad , \quad X_{LA} = Z_A - R \quad , \quad L_A = X_{LA} / (2\pi f)$$

Similarly for the second case

$$Z_B = V_2 / I_2 \quad , \quad X_{LB} = Z_B - R \quad , \quad L_B = X_{LB} / (2\pi f)$$

$$\left(\frac{L_1}{L_2}\right) = \left(\frac{N_1}{N_2}\right)^2 = \left(\frac{230}{115}\right)^2 = 4$$

$$L_1 = 4L_2$$

$$L_2 = \frac{L_A - 2M}{5}$$

From the above equations  $L_1$  ,  $L_2$  ,  $M$  and  $k$  can be found out. The experimental determinations of the above parameters are carried out for a pair of transformer winding.

**Sample Calculation**

For Aiding flux circuit  $V_A = V_{A1} + V_{A2}$

For opposing flux circuit  $V_B = V_{B1} - V_{B2}$

Resistance of transformer winding  $R = \dots\dots\dots$

Applied voltage for aiding circuit  $V_A = \dots\dots\dots$

Applied current for aiding circuit  $I_A = \dots\dots\dots$

Applied voltage for opposing circuit  $V_B = \dots\dots\dots$

Applied current for opposing circuit  $I_B = \dots\dots\dots$

$Z_A = (V_A / I_A) = \dots\dots\dots$

$X_{LA} = (Z_A^2 - R^2)^{1/2} = \dots\dots\dots$

$L_A = X_{LA} / (2\pi f) = \dots\dots\dots$

$Z_B = (V_B / I_B) = \dots\dots\dots$

$X_{LB} = (Z_B^2 - R^2)^{1/2} = \dots\dots\dots$

$L_B = X_{LB} / (2\pi f) = \dots\dots\dots$

Mutual inductance  $M = (L_A - L_B) / 4 = \dots\dots\dots$

$L_2 = \frac{L_A - 2M}{5} = \dots\dots\dots$

$L_1 = 4L_2 = \dots\dots\dots$

$k = M / (L_1 L_2)^{1/2} = \dots\dots\dots$



## **Procedure**

### ***For aiding flux circuit:***

1. Connections are made as shown in the first figure(Aiding flux circuit).
2. Supply is switched on with autotransformer in the minimum position.
3. The autotransformer is adjusted to get the rated voltage in voltmeter  $V_A$ .
4. The corresponding readings in all meters are noted down. In this case the fluxes produced by both the coils are additive in nature (ie,  $V_A = V_{A1} + V_{A2}$ ).
5. Adjust the auto transformer to minimum position and switch of supply.

### ***For opposing flux circuit:***

1. Connections are made as shown in the second figure(Opposing flux circuit)
2. Supply is switched on with autotransformer in the minimum position.
3. The fluxes produced by the two coils are now in subtractive polarity (ie,  $V_B = V_{B1} - V_{B2}$ ).
4. Adjust the auto transformer till the voltmeter  $V_{B1}$  reading equal to  $V_{A1}$  reading of flux aiding circuit.
5. This is done to maintain the same flux in both the cases.
6. The readings of all meters are noted down and tabulated.
7. Adjust the auto transformer to minimum position and switch of supply.

## **Result**

Determined the self inductance, mutual inductance and coupling coefficient of the given iron cored transformer windings.

































































