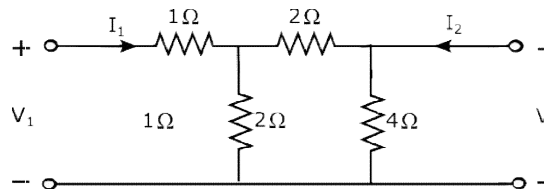



**PART C**

*Answer any two full questions, each carries 20 marks*


- 7 a) Differentiate between self-inductance and mutual inductance. (2)
- b) Give the expressions of quality factor of series and parallel RLC networks. (3)
- c) Find the ABCD parameters of the network shown. (7)



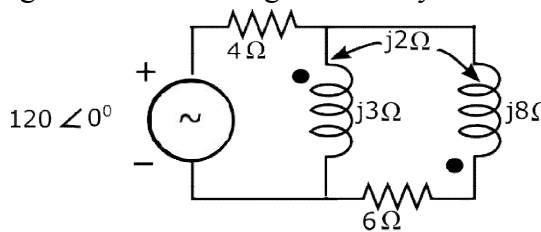- d) Find the current through 6Ω resistor using mesh analysis. (8)



- 8 a) Explain the term selectivity. (2)
- b) Draw the series and parallel connection of two port network and derive the parameter matrices for the resultant network. (8)
- c) Draw the circuit of a single tuned circuit and derive an expression for output voltage. (10)
- 9 a) Explain the following terms and write the relation between them: (4)
  - i) Bandwidth
  - ii) Q factor.
- b) Find the drop across 5 Ω resistor. (6)

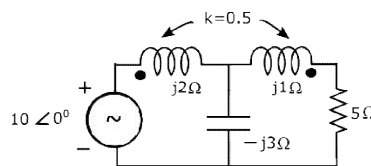

- c) Currents  $I_1$  and  $I_2$  entering at port 1 and port 2 respectively of a two-port network are given by (10)

$$I_1 = 0.5V_1 - 0.2V_2$$

$$I_2 = -0.2V_1 + V_2$$

Find Y, Z and ABCD parameters. From Y parameters, check whether the network is reciprocal and symmetrical.

\*\*\*\*