

D 2338

(Pages 2)

Name.....

Reg. No.....

THIRD SEMESTER B.TECH. (ENGINEERING) DEGREE  
EXAMINATION, DECEMBER 2009

CS/IT 04 305—SWITCHING THEORY AND LOGIC DESIGN

(2004 Admissions)

Time : Three Hours

Maximum : 100 Marks

- I. (a) Write a brief note on self dual function.  
(b) Differentiate between normal and canonical forms with the help of examples.  
(c) Implement the logic function  $Y = AB + A\bar{C}$  using NAND gates only.  
(d) Explain the difference between a multiplexer and demultiplexer.  
(e) Discuss the importance of testing in digital circuit design.  
(f) Explain about the essential prime cube theorem.  
(g) Explain the basic difference between a latch and a Flip-Flop.  
(h) Write a brief note on ripple counters.

(8 × 5) = 40 marks

- II. (a) Reduce the following function using Quine McClusky method :

$$F(A, B, C, D, E) = \sum (0, 1, 2, 8, 9, 15, 17, 21, 24, 25, 27, 31)$$

(15 marks)

Or

- (b) (i) Simplify the following expression using K-Map :

$$F(A, B, C, D) = \sum (1, 5, 7, 8, 9, 10, 11, 14, 15)$$

(8 marks)

- (ii) Write short notes on switching Algebra.

(7 marks)

- III. (a) Explain about encoders and decoders in detail.

(15 marks)

Or

- (b) Explain the principle of operation of parallel adder and look ahead adder.

(15 marks)

- IV. (a) Discuss about the Fault Tolerant techniques.

(15 marks)

Or

Turn over