

C 15644

(Pages : 2)

Name.....

Reg. No.....

**FOURTH SEMESTER B.TECH. (ENGINEERING) DEGREE
EXAMINATION, JUNE 2011**

EE 09 405/PTEE 09 404—DIGITAL ELECTRONICS

(2009 Admissions)

Time : Three Hours

Maximum : 70 Marks

Part A

1. Define Propagation Delay.
2. Give the truth table of NAND and XNOR gate.
3. Differentiate between Combinational logic circuit and Sequential logic circuit.
4. How is JK FF converted to T FF ?
5. What is the function of program counter ?

(5 × 2 = 10 marks)

Part B

6. Compare CMOS and TTL technologies based on power dissipation voltage levels, noise immunity.
7. Perform the following operations in two's complement form :
 - (i) $-36_H + 4D_H$
 - (ii) $-AF_H - 6C_H$
8. Draw the circuit of a full adder along with truth table.
9. Explain the 4-bit comparator circuit.
10. Draw and explain a static RAM cell and a dynamic RAM cell.
11. List the salient features of 8085 microprocessor.

(4 × 5 = 20 marks)

Part C

12. (a) Discuss the operation of CMOS inverter circuit with characteristics.

Or

- (b) Explain the schematic of 3 input TTL NAND gate.

13. (a) Construct a truth table for BCD to gray code converter and draw the simplified circuit schematic (Use Karnaugh map).

Or

- (b) (i) Differentiate between ROM, PLA and PAL. (4 marks)
- (ii) Implement a 4×1 multiplexer in the above 3 methods. (6 marks)

Turn over

14. (a) Explain the operation of bidirectional shift register.

Or

(b) Design a synchronous counter for the state diagram given below :



Use D flip-flop.

15. (a) (i) Discuss the basic microcomputer operations.
(ii) What are the various flags available and state their uses.

Or

(b) Write the VHDL code, using structural modelling for a full subtractor.

(4 × 10 = 40 marks)